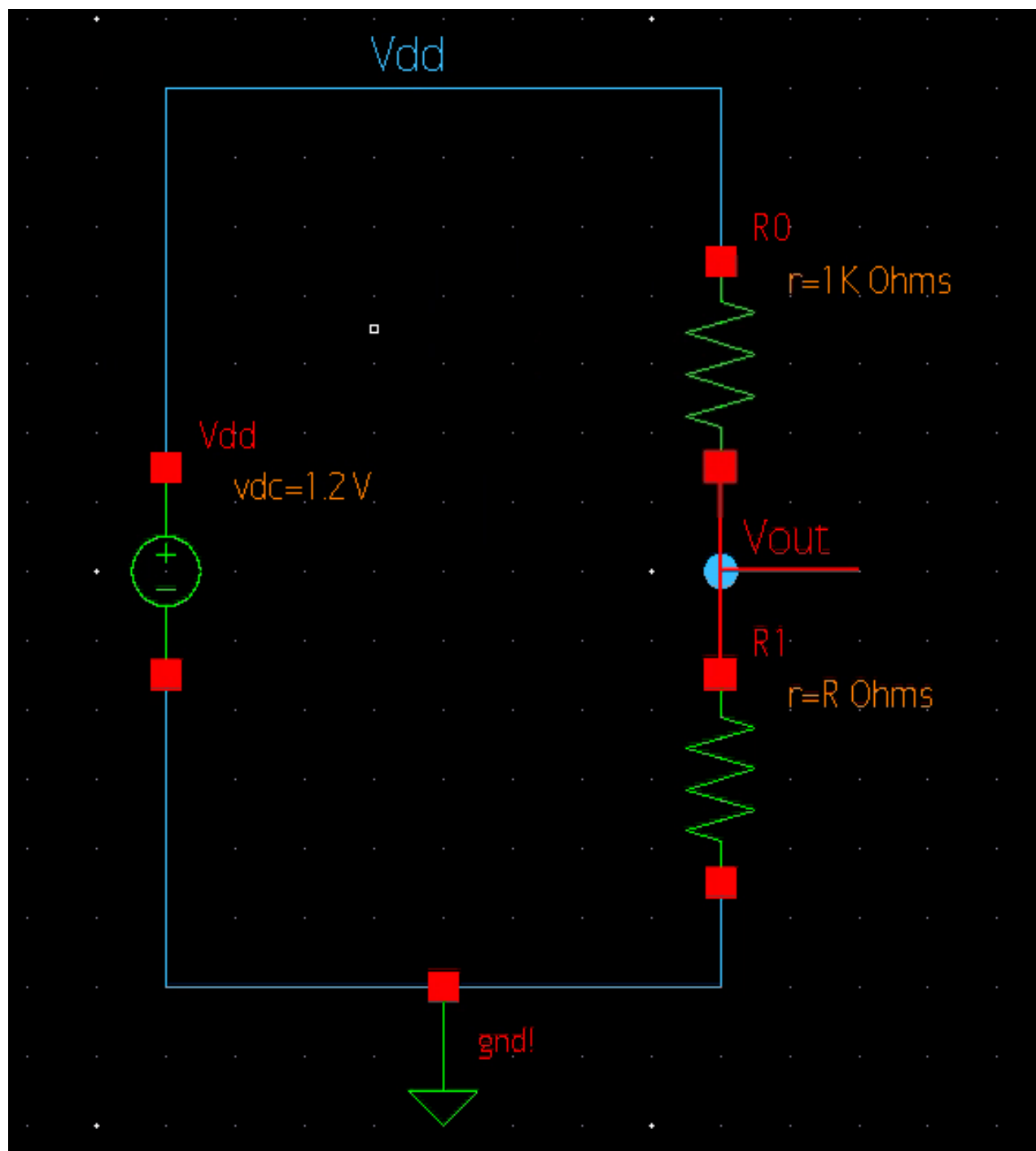


Lab 1: Introduction to Synopsys
by Joseph Yu

Procedure:

Part A: Complete!

Part B:



(Next Page)

Source Sweep:

"Vout" is equal to half of "Vdd" for all listed values.

Session Setup Variables Outputs Simulation Results Tools Window Help

Testbench: default History Point: 1

Status: Simulation Completed HSPICE

| Variable | Value |
|--------------|-------|
| temp | 25 |
| R | 1k |
| Click to add | |


| Analysis | Type | En | Value |
|------------|--------------|-------------------------------------|--|
| dc | dc | <input checked="" type="checkbox"/> | Sweep Variable: Source Source Name: /Vdd |
| useCard | | <input type="checkbox"/> | |
| card | | | |
| sweep | Source | | |
| source | /Vdd | | |
| sweepType | Linear Steps | | |
| hysteresis | | <input type="checkbox"/> | |
| start | 0 | | |
| stop | 1.2 | | |
| stepSize | 0.01 | | |

Variable Set: default

Outputs Specifications Scatter Histogram Q-Q Parametric Reduction

| Output | Expression | Value | Analyses | Plot Color |
|--------------|------------|-------|----------|------------|
| | v(/Vout) | | dc | |
| Click to add | | | | |

 Output Set: default ☒ Import Measures ☒ Group Signals Plotting Mode: replace Plot Clear



(Next Page)

Resistance Sweep:

When "R" is zero ohms, "Vout" is (apparently) zero volts.

When "R" is 100k ohms, "Vout" is almost equal to the set "Vdd", which is 1.2 volts.

Testbench: default History Point: 1

Status: Simulation Completed HSPICE ☐ History

| Variable | Value |
|--------------|-------|
| temp | 25 |
| R | 1k |
| Click to add | |


| Analysis | Type | En | Value |
|------------|------|-------------------------------------|--|
| dc | dc | <input checked="" type="checkbox"/> | Sweep Variable: Design Variable Variable Name: R |
| useCard | | <input type="checkbox"/> | |
| card | | | |
| sweep | | | Design Variable |
| designVar | | | R |
| sweepType | | | Linear Steps |
| hysteresis | | <input type="checkbox"/> | |
| start | | | 0 |
| stop | | | 100k |
| stepSize | | | 1k |

Variable Set: default

Outputs Specifications Scatter Histogram Q-Q Parametric Reduction


| Output | Expression | Value | Analyses | Plot Color |
|--------------|------------|-------|----------|---|
| | v(/Vout) | | dc | <input checked="" type="checkbox"/> <input checked="" type="checkbox"/> <input checked="" type="checkbox"/> |
| Click to add | | | | |

 Output Set: default ☒ Import Measures ☒ Group Signals Plotting Mode: replace Plot Clear




(Next Page)

Part C:

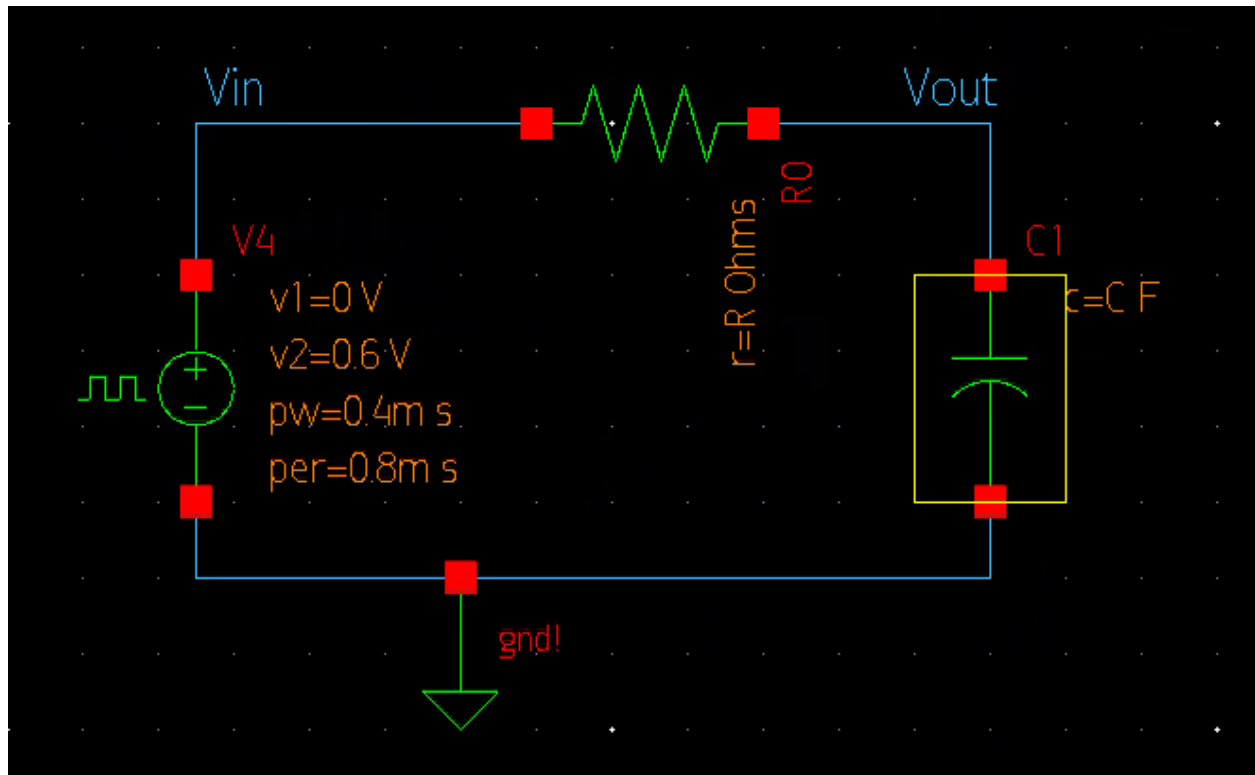

Resistance:

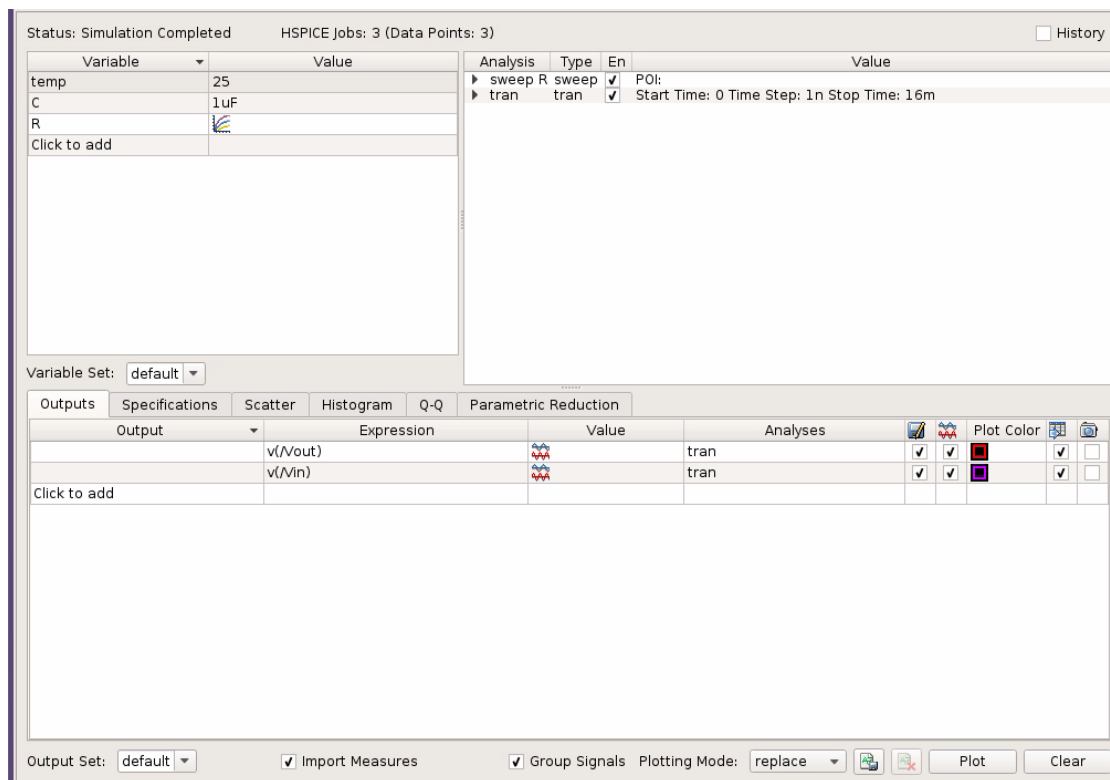(Measure tool values should be in the graph on the next page.)



(Next Page)



Rise and fall time measures the amount of time it takes for a wave to deviate (through rising or falling) from 10% to 90% of the distance traveled.

In the third case ($R = 10k\Omega$), the value never falls more than 90% of the height of the last wave, so the wave essentially continues to rise indefinitely. Therefore, the rise time is technically infinite, and the fall time doesn't exist.

Capacitance:
(Measurements in the graph below).

Status: Simulation Completed HSPICE Jobs: 3 (Data Points: 3) ☐ History


| Variable | Value |
|--------------|-------------|
| temp | 25 |
| C | |
| R | 1k Ω |
| Click to add | |

| Analysis | Type | En | Value |
|--------------|-------|-------------------------------------|--|
| sweep C | sweep | <input checked="" type="checkbox"/> | POI: |
| rangeType | | | POI |
| poi | | | 0.01 0.1 1 |
| stepType | | | Linear |
| linearPoints | | | |
| tran | tran | <input checked="" type="checkbox"/> | Start Time: 0 Time Step: 1n Stop Time: 16m |
| useCard | | | <input type="checkbox"/> |
| card | | | |
| start | | | 0 |
| uic | | | <input type="checkbox"/> |
| numIntervals | | | 1 |
| step | | | 1n |
| stop | | | 16m |

Variable Set: default

| Output | Expression | Value | Analyses | Plot Color |
|--------------|------------|-------|----------|-------------------------------------|
| | v(/Vout) | | tran | <input checked="" type="checkbox"/> |
| | v(/Vin) | | tran | <input checked="" type="checkbox"/> |
| Click to add | | | | |


 
Output Set: default ☒ Import Measures ☒ Group Signals Plotting Mode: replace Plot Clear






ELEN 153L Lab Report 2

by Joseph Yu


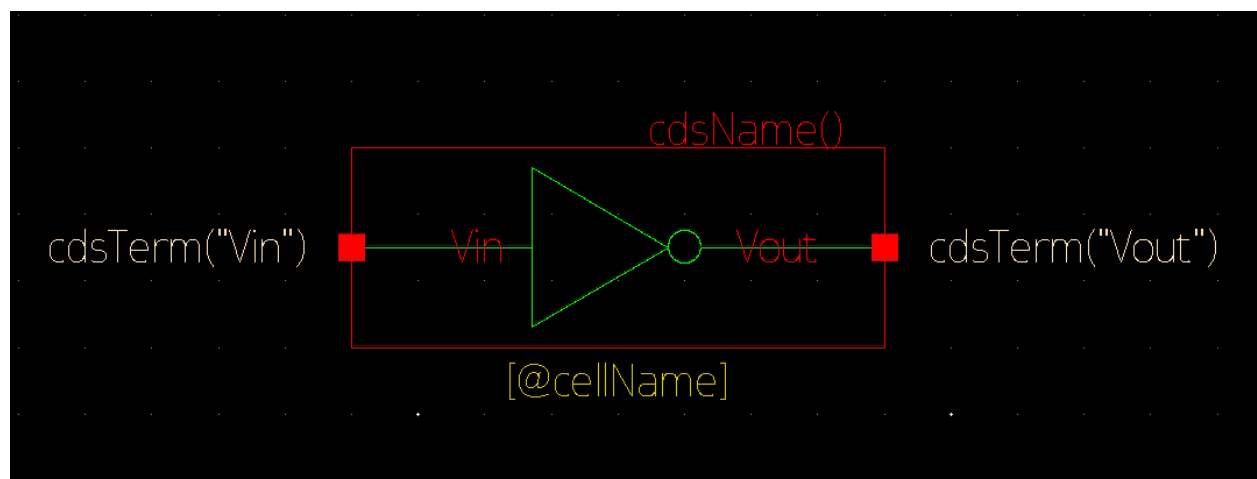
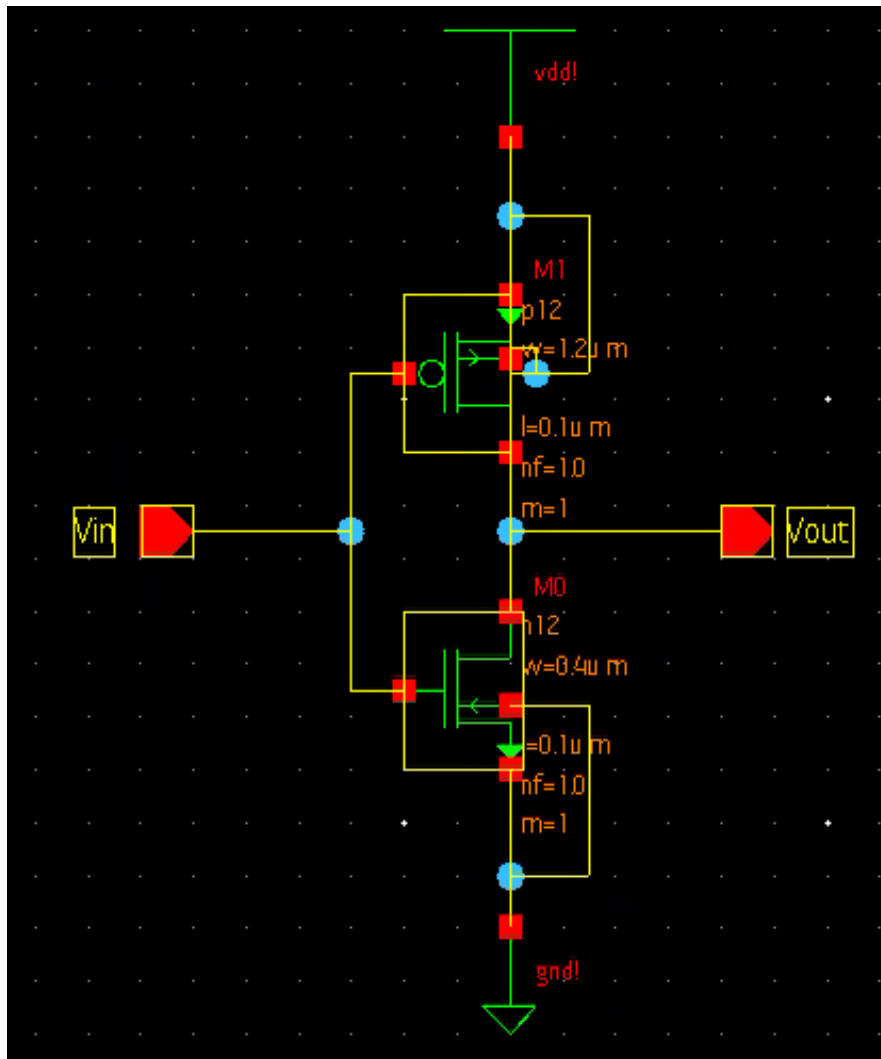
Inverter Schematic/ Symbol (Answers to Lab Questions on Page 6)



VTC

 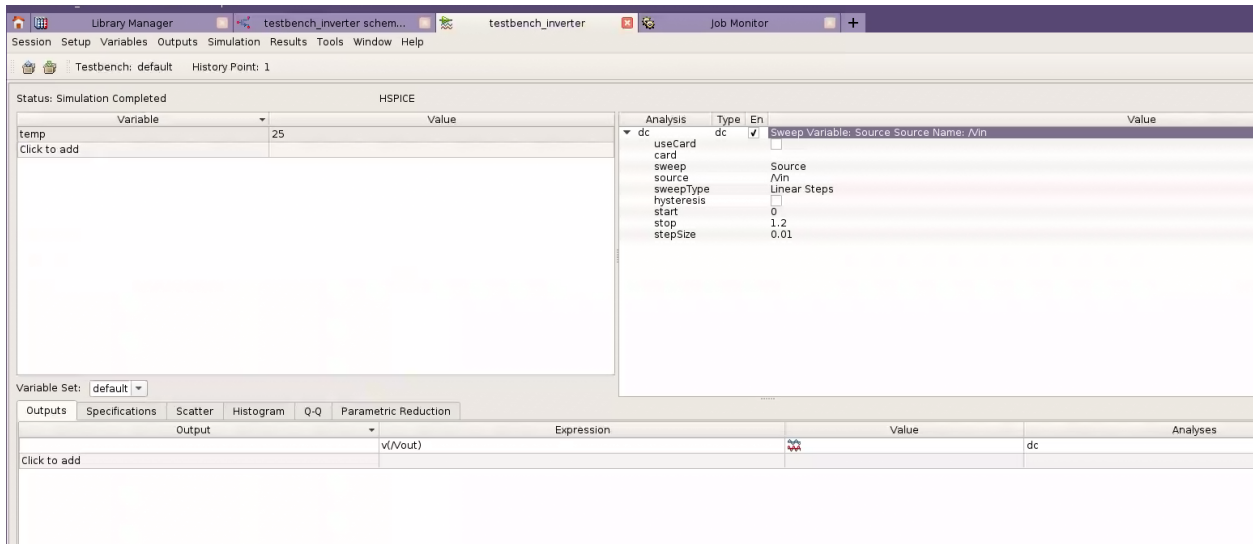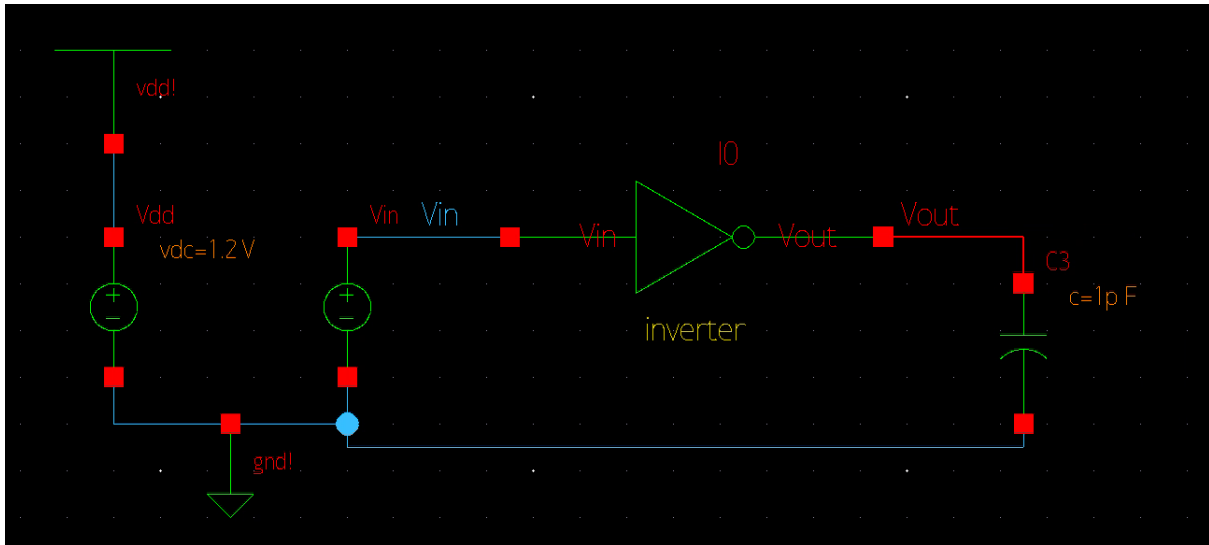

VTC OP

   


| Filter results... X Advanced sorting... X (Showing 2 of 2) Show Advanced Filters | | | | | | | | | | | | | | | | | | | |
|--|-----------|-----------|-----------|-----------|----------|----------|-----------|----------|-----------|-----------|-----------|--------|-----|-----------|-----------|----------|-----------|-----------|--|
| ftot | cgd | cgs | cgtot | cstot | gam eff | gds | gm | gmb | lbd | lbs | ld | region | vbs | vds | vdstat | vgs | vod | vth | |
| 183f | 0.128835f | 0.185905f | 0.394796f | 0.505261f | 0.400000 | 6.35057n | 0.107932u | 28.5056n | -1.21000p | 1.22233y | 4.04770n | 3 | 0 | 1.20000 | 39.5863m | 0 | -0.334679 | 0.334679 | |
| 20f | 1.14204f | 1.38204f | 2.50792f | 1.85194f | 0.400000 | 1.16853m | 2.76169n | 1.33826n | 5.88202a | -15.2330y | -4.94771n | 1 | 0 | -4.23413u | -0.660053 | -1.20000 | -0.921972 | -0.278028 | |

| CAP MOS NET VSRC Filter results... X Advanced sorting... X (Showing 2 of 2) Show Advanced Filters | | | | | | | | | | | | | | | | | | | |
|---|----------|------|----------|-----------|-----------|-----------|-----------|-----------|-----------|----------|----------|-----------|----------|-----------|-----------|-----------|--------|----|--|
| name | analysis | time | beta | cbtot | cdtot | cgd | cgs | cgtot | cstot | gam eff | gds | gm | gmb | lbd | lbs | ld | region | vb | |
| 10/M0 | op | 0 | 7.30851m | 0.553565f | 0.282983f | 0.128835f | 0.185905f | 0.394796f | 0.505261f | 0.400000 | 6.35057n | 0.107932u | 28.5056n | -1.21000p | 1.22233y | 4.04770n | 3 | 0 | |
| 10/M1 | op | 0 | 1.60261m | 1.77894f | 2.25620f | 1.14204f | 1.38204f | 2.50792f | 1.85194f | 0.400000 | 1.16853m | 2.76169n | 1.33826n | 5.88202a | -15.2330y | -4.94771n | 1 | 0 | |

(Next Page)

Transient

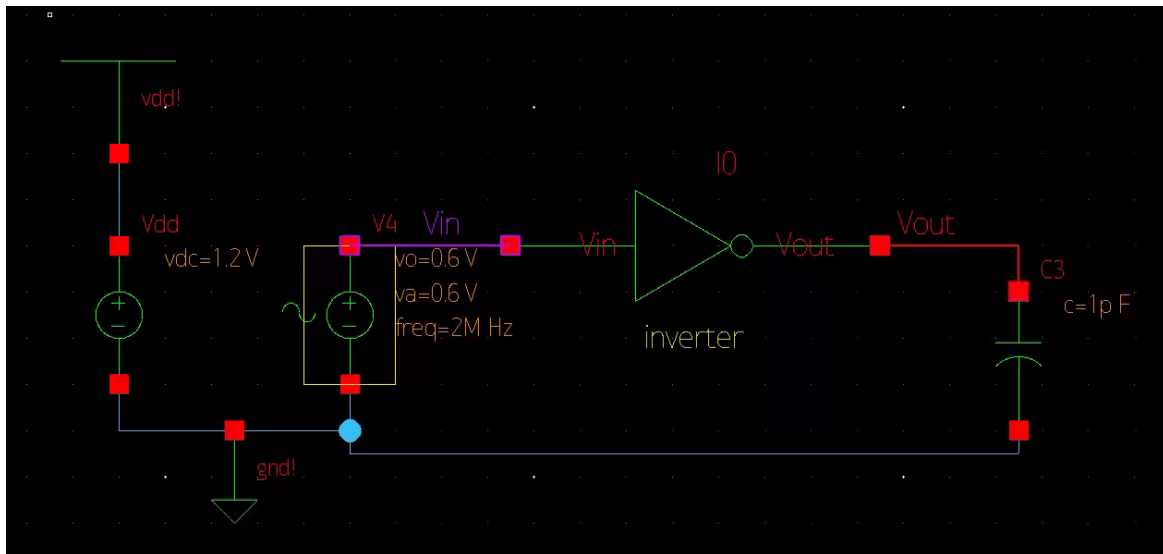

Testbench/State: HSPICE_default History Point: 1

Status: Simulation Completed HSPICE

| Variable | Value |
|----------|-------|
| temp | 25 |

Click to add


Analysis Type En

- dc dc ☒ Sweep Variable: Source Source Name: /Vin
- tran tran ☒ Start Time: 0 Time Step: 10n Stop Time: 1u

Variable Set: default

| Output | Expression | Value |
|--------|------------|-------|
| | v(Vout) | |
| | v(Vin) | |
| | f | |

Click to add

 

Lab Questions:

Step 3 in Lab Procedure:

> $V_m = 0.631 \text{ V}$

> $V_{out} = -1 \rightarrow V_{in} = 0.519, 0.725$

Questions concerning Lab Procedure:

a) NMOS: length = 0.1 μm (micrometers), width = 0.4 μm

PMOS: length = 0.1 μm , width = 1.2 μm

b) $V_m = 0.631 \text{ V}$

$V_{oh} = 1.09 \text{ V}$

$V_{il} = 0.519 \text{ V}$

$V_{ol} = 0.107 \text{ V}$

$V_{ih} = 0.725 \text{ V}$


(Screenshots on page 3)

Conclusions:

In this lab, we created a symbol for the logical negator using a PMOS and a NMOS in Synopsys Custom Compiler and performed some simulations (VTC and transient) using the new symbol.

The intricacies and challenges that we faced during the lab allowed us to adapt to the new software and understand the relations between logical gates and the semiconductor transistors they are composed of.

[ELEN153L] Lab Report 3
by Joseph Yu

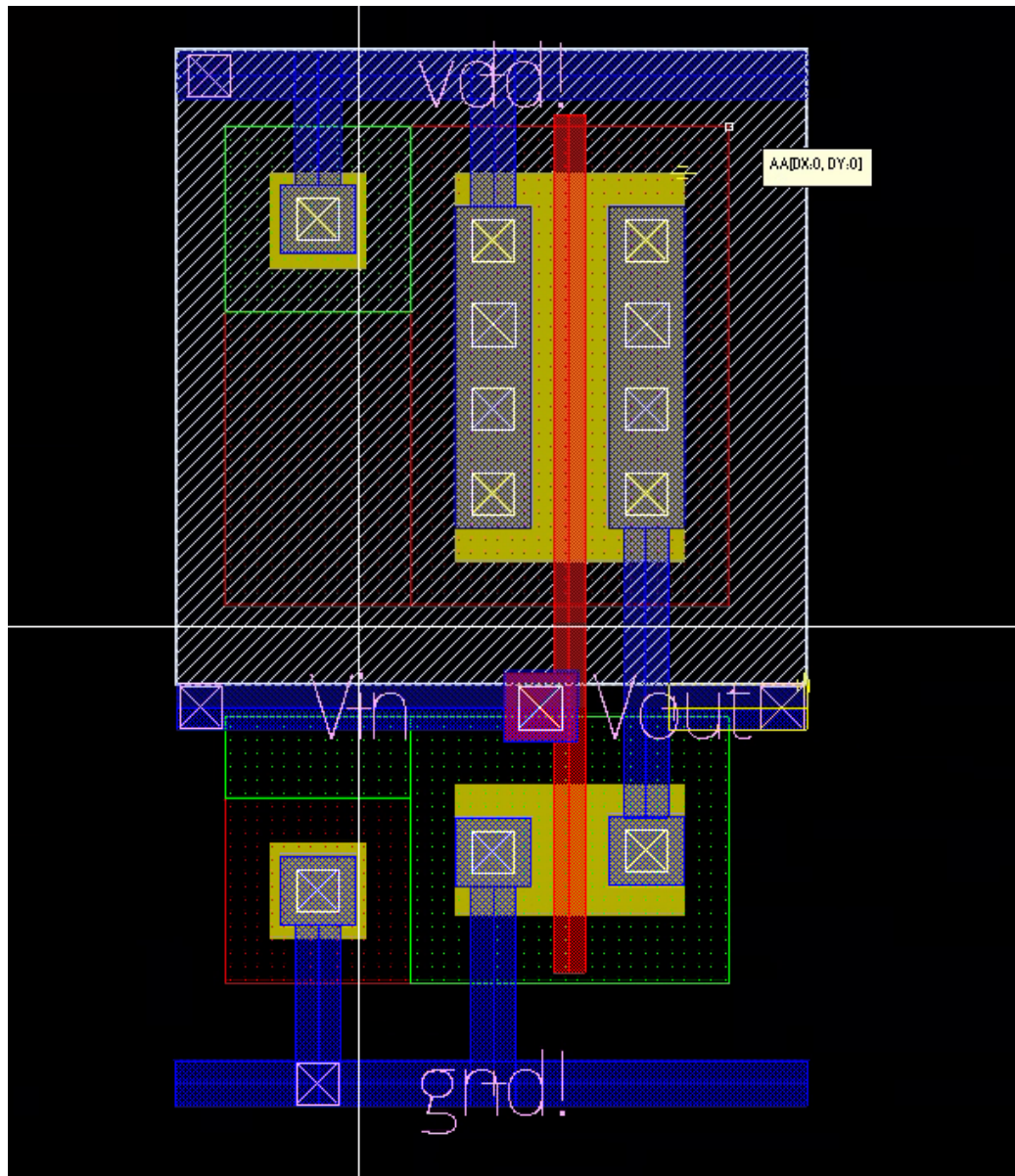

Procedure Step 1:

1.

NWELL: N-Well.
NIMP: N+ Implantation
PIMP: P+ Implantation
DIFF: Diffusion
PO: Poly Silicon

M1: Metal 1
M2: Metal 2
DIFFCON: Diffusion Contact
POLYCON: Poly Contact

2. Length (Y-Axis) = 0.1 μm
PMOS, NMOS Width (X-Axis) = 1.2 μm , 0.4 μm

(Next Page)

run_icv.shrules.lvs.9m_saed90_lvs.lvs.rsinverter.lvs.custom_compiler.rcinverter.RESULTSinverter.LAYOUT_ERRORSinverter.LVS_ERRORSstdout.lvs.log

LAYOUT ERRORS RESULTS: CLEAN

#####

Library name: ELEN53
Structure name: inverter
Generated by: IC Validator RHEL64 Q-2019.12-SP1-1.5351723 2020/02/24
Runset name: /DCNFS/users/student/jyu4/ELEN53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs/rules.lvs.9m_saed90_lvs.lvs.rs
User name: jyu4
Time started: 2023/10/13 04:26:00PM
Time ended: 2023/10/13 04:26:14PM

Called as: icv -f openaccess -i ELEN53 -c inverter -oa view layout -oa lib_defs /DCNFS/users/student/jyu4/ELEN53/lib_defs -oa 1
ayer_map /DCNFS/applications/synopsys/2019/app/SAED/SAED_PDK90m/techfiles/saed_pdk90_layer_map -rc /DCNFS/users/student/jyu4/ELE
N53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs/inverter.lvs.custom_compiler.rc -s /DCNFS/users/student/jyu4/ELEN53/synopsys
_custom/pvjob_ELEN53.inverter.icv.lvs/inverter.custom_compiler.sp -sf SPICE -stc inverter -sf SPICE -vue /DCNFS/users/student/jy
u4/ELEN53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs/rules.lvs.9m_saed90_lvs.lvs.rs

Find:NextPrevious

Console
SAED PDK 90: Loaded display resources
Error: Error returned from command de::addPoint (0.0.14) -relative true'. (TCL)
Error: Error returned from command de::addPoint (0.14 0.14) -relative true'. (TCL)
Warning: Could not commit in this state. Please provide a point to commit. (LE_CREATE_INTERCONNECT-011)
Warning: No default viaDef available. (LE_CREATE_INTERCONNECT-008)
Warning: No default viaDef available. (LE_CREATE_INTERCONNECT-008)
Warning: No default viaDef available. (LE_CREATE_INTERCONNECT-008)
Warning: No default viaDef available. (LE_CREATE_INTERCONNECT-008)
Information:
JobID: icv drc 1
Completed with no errors
Information: -Starttime.netlist:for:action:"ELEN53/inverter/schematic" -"/NETLISTING.M1"

run_icv.shrules.lvs.9m_saed90_lvs.lvs.rsinverter.lvs.custom_compiler.rcinverter.RESULTSinverter.LAYOUT_ERRORSinverter.LVS_ERRORSstdout.lvs.log

ICV_Compare (R) Hierarchical Layout Vs. Schematic
RHEL64 Q-2019.12-SP1-1.5351723 2020/02/24
Copyright (C) Synopsys, Inc. All rights reserved.

LVS error file = inverter.LVS_ERRORS
Layout error file = inverter.LAYOUT_ERRORS
Schematic netlist = /DCNFS/users/student/jyu4/ELEN53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs/inverter.sch_out
Layout netlist = /DCNFS/users/student/jyu4/ELEN53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs/inverter.net
Runset file = /DCNFS/users/student/jyu4/ELEN53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs/rules.lvs.9m_saed90_lvs.lvs.rs
Working directory = /DCNFS/users/student/jyu4/ELEN53/synopsys_custom/pvjob_ELEN53.inverter.icv.lvs
Compare directory = run_details/compare
Compare start time = 2023-10-13 16:26:11

Final comparison result:PASS


TOP equivalence point: [inverter, inverter]

Comparison summary
1 Successful equivalence points
0 Failed equivalence points

Find:NextPreviousMatch Case

Console
JobID: icv_lvs 1
--- Error Summary ---
Compare Error Summary
Refer to inverter.LVS_ERRORS.
LVS compare Result:PASS
TOP equivalence point: [inverter, inverter]
1 Successful equivalence points
0 Failed equivalence points
Information: Connection established with 'IC Validator VUE' running on 'linux22404.dc.engr.scu.edu'.
>

(Next Page)


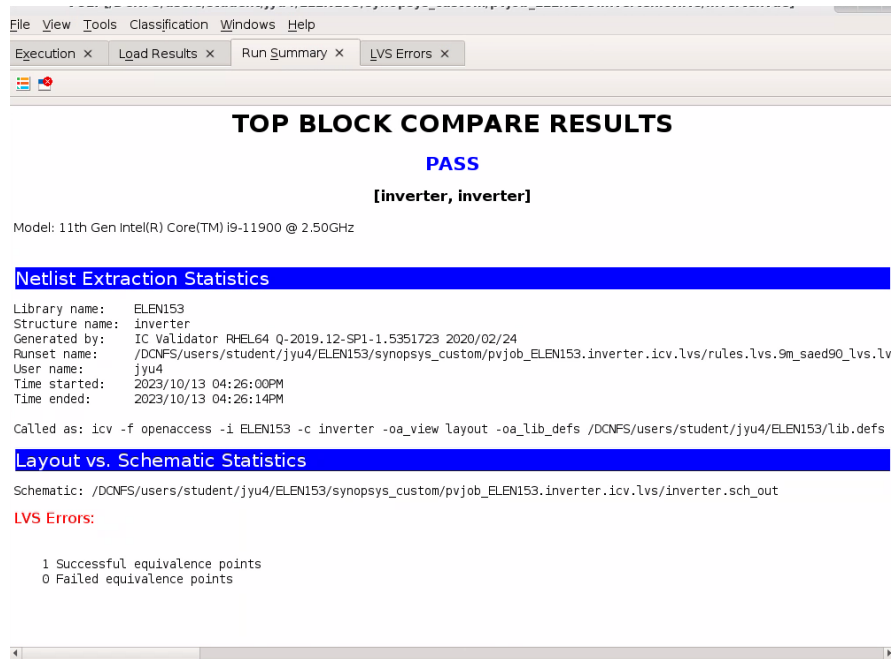


Conclusion:




Today, I was able to create the layout of an inverter in Synopsis Lab. It was able to pass all verification tests and further familiarize me with the inner workings of logical gates in relation to its metallic and transistor components. Nothing terrible happened.


Lab 4 Report
by Joseph Yu

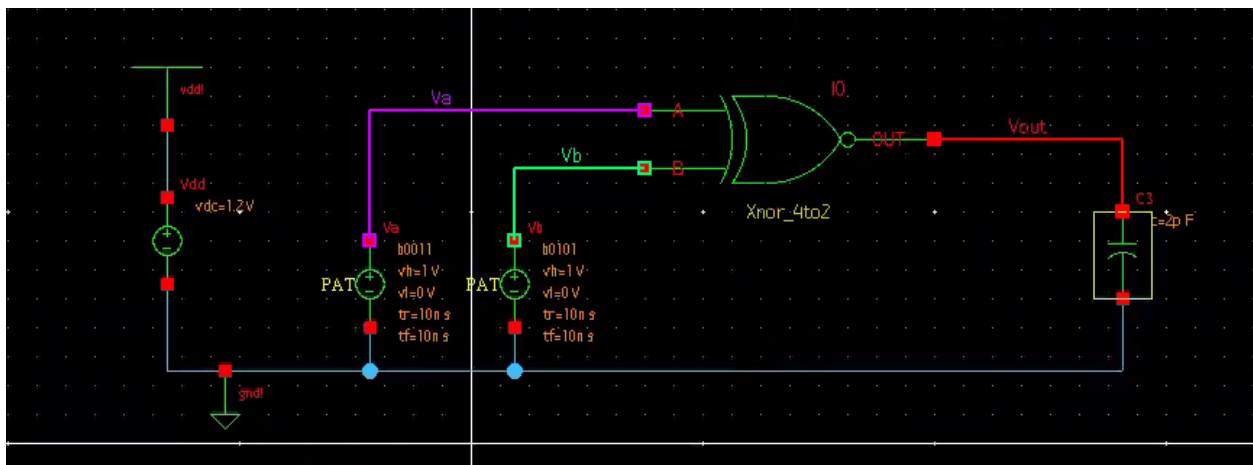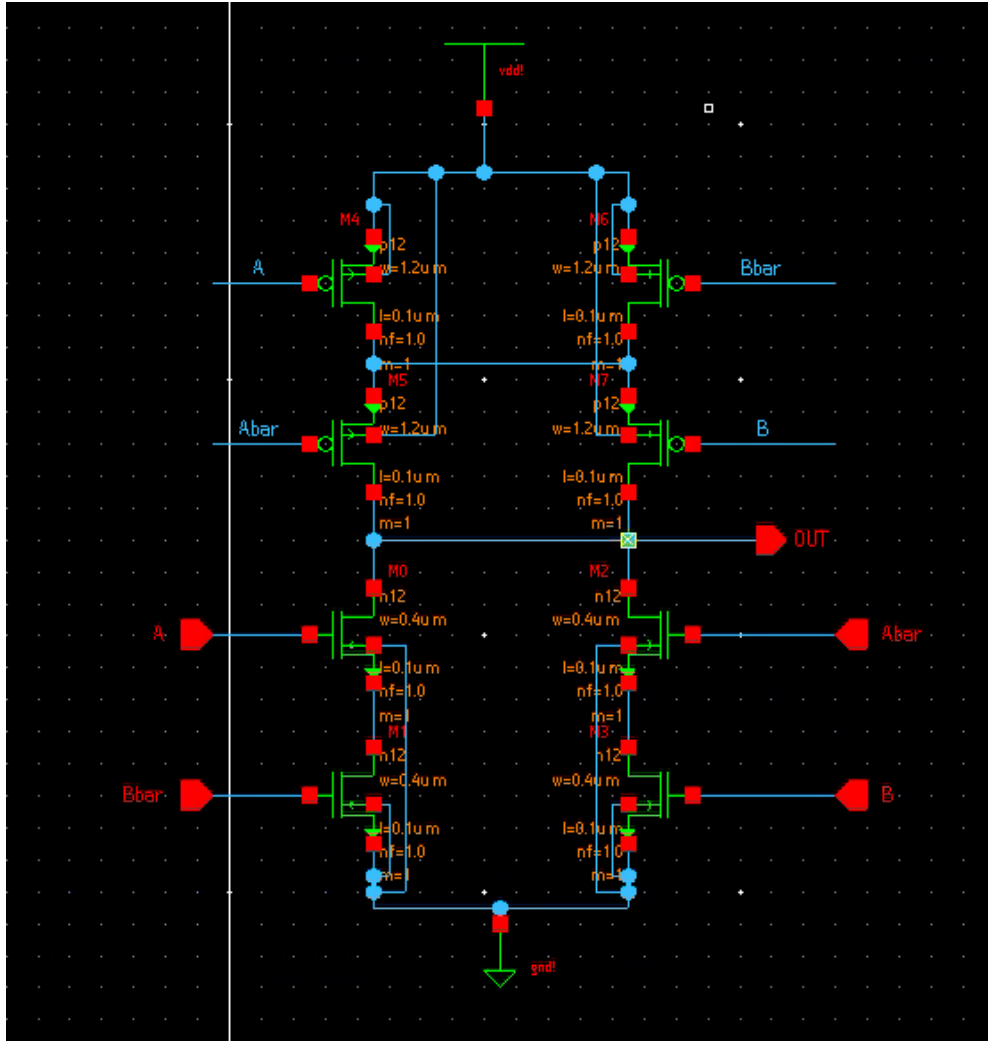Pictures: (Answer to Procedure Questions on Page 4)



(Next Page)

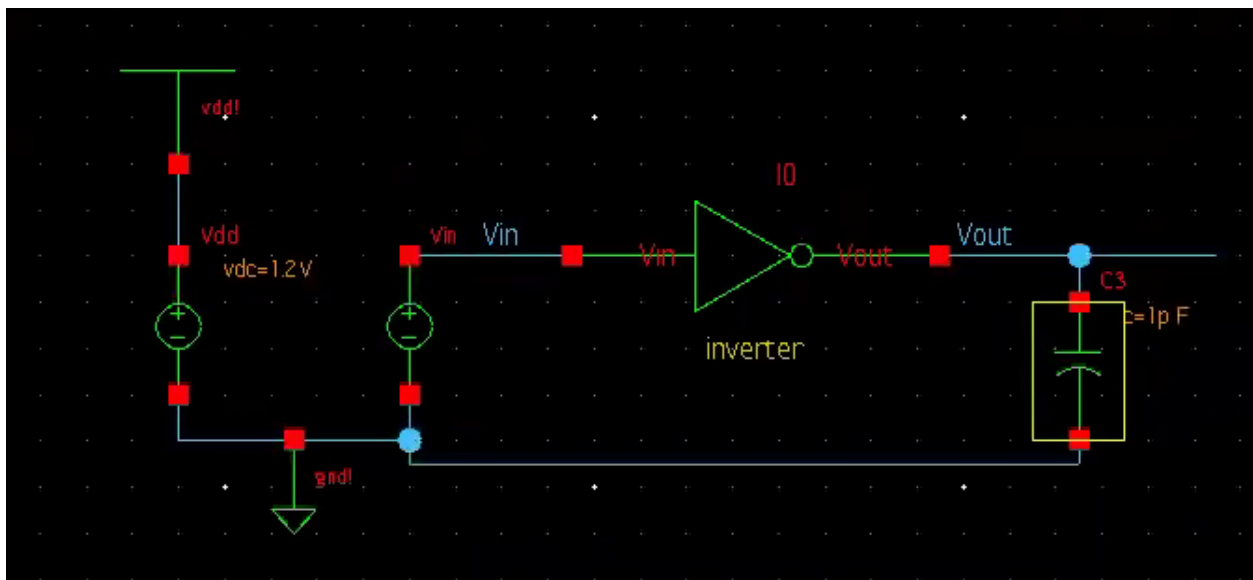 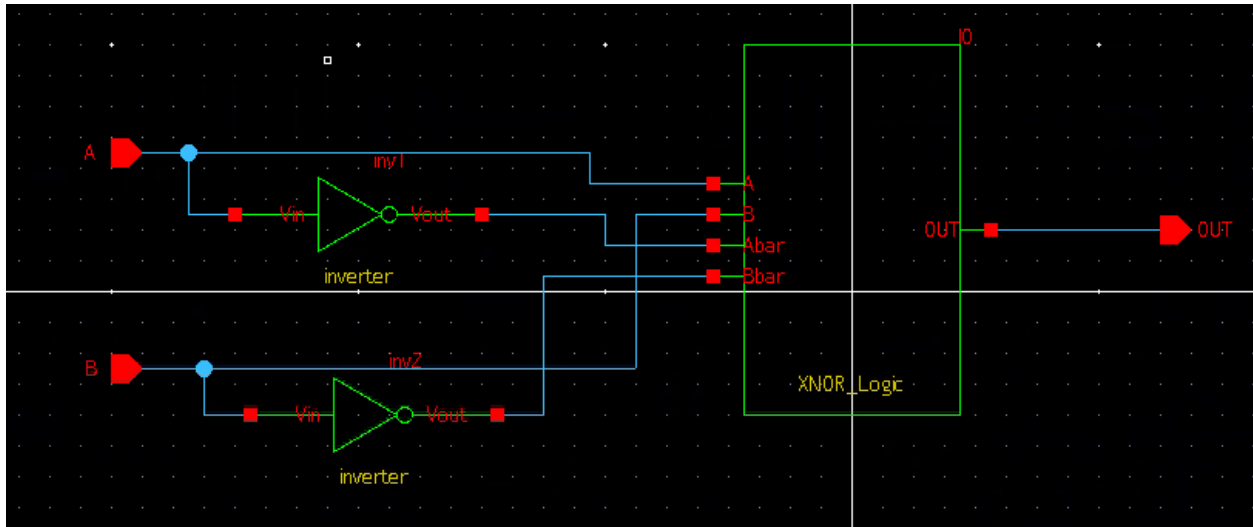

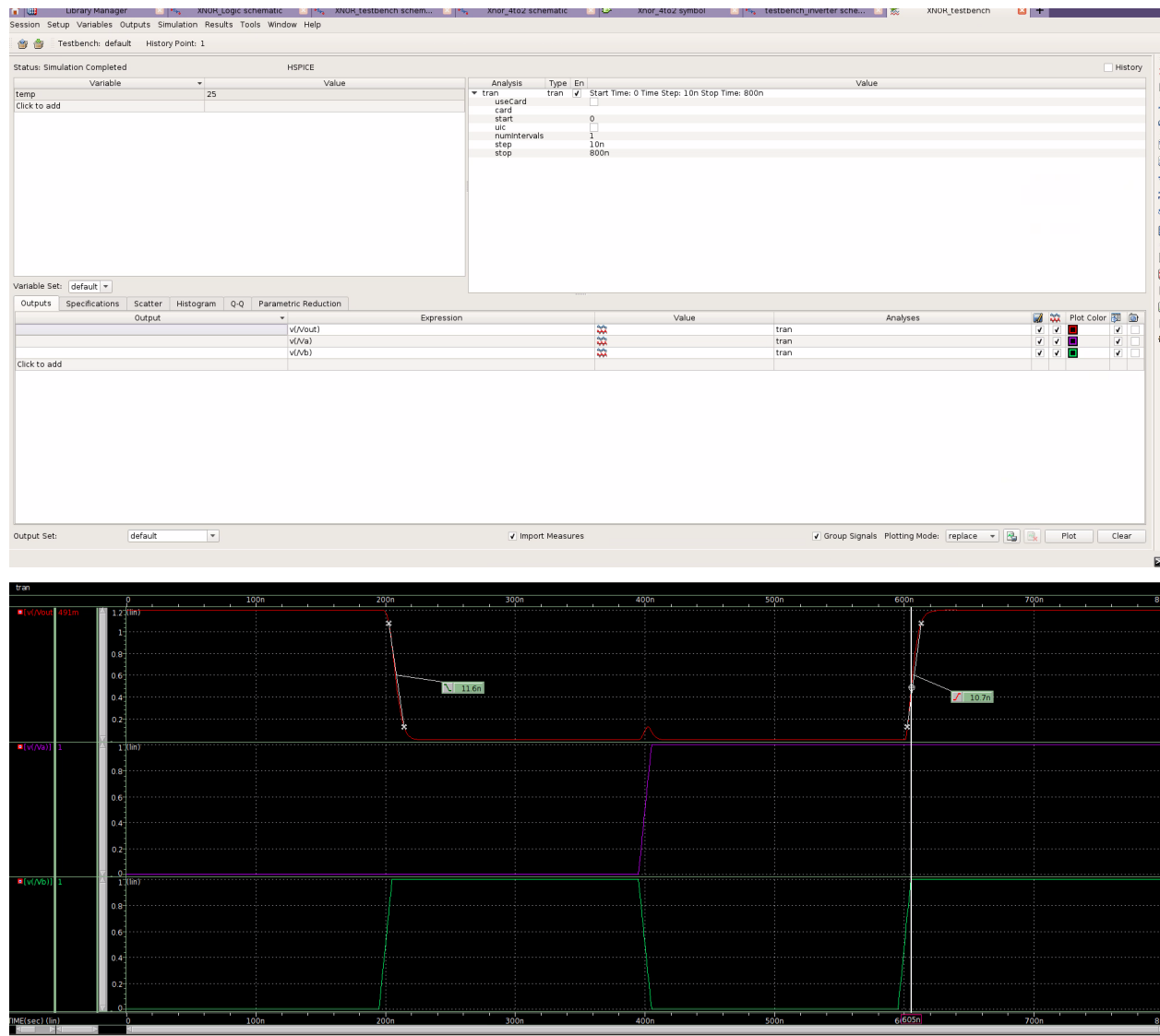

(Caption: Above measurements depicted are 11.6 ns and 10.7 ns)

(Next Page)

Questions:

Part C:

Fall: 11.6 ns

Rise: 10.7 ns (Refer to Page 3)

| | | | | |
|------------|--------------------------------|-----------------------------------|--------------------|--------------------------|
| run_icv.sh | rules.drc.9m_saed90_icv.drc.rs | XNOR_Logic.drc.custom_compiler.rc | XNOR_Logic.RESULTS | XNOR_Logic.LAYOUT_ERRORS |
|------------|--------------------------------|-----------------------------------|--------------------|--------------------------|

System Startup Time=0:00:00 User=0.00 Sys=0.02 Mem=0.437 GB

Command execution begins. Details recorded in the summary and log files:

/DCNFS/users/student/jyu4/ELEN153/synopsys_custom/pvjob_Lab4.XNOR_Logic.icv.drc/run_details/XNOR_Logic.sum

/DCNFS/users/student/jyu4/ELEN153/synopsys_custom/pvjob_Lab4.XNOR_Logic.icv.drc/run_details/rules.drc.9m_saed90_icv.drc.dp.

g

Running ...

| | | |
|-------------------|----------------|----------------------|
| ICV_Engine run is | 1% complete. | Elapsed Time=0:00:00 |
| ICV_Engine run is | 2% complete. | Elapsed Time=0:00:01 |
| ICV_Engine run is | 3% complete. | Elapsed Time=0:00:03 |
| ICV_Engine run is | 4% complete. | Elapsed Time=0:00:03 |
| ICV_Engine run is | 5% complete. | Elapsed Time=0:00:03 |
| ICV_Engine run is | 10% complete. | Elapsed Time=0:00:03 |
| ICV_Engine run is | 15% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 20% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 25% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 30% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 35% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 40% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 45% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 50% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 55% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 60% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 65% complete. | Elapsed Time=0:00:04 |
| ICV_Engine run is | 70% complete. | Elapsed Time=0:00:05 |
| ICV_Engine run is | 75% complete. | Elapsed Time=0:00:05 |
| ICV_Engine run is | 80% complete. | Elapsed Time=0:00:05 |
| ICV_Engine run is | 85% complete. | Elapsed Time=0:00:05 |
| ICV_Engine run is | 90% complete. | Elapsed Time=0:00:05 |
| ICV_Engine run is | 95% complete. | Elapsed Time=0:00:06 |
| ICV_Engine run is | 100% complete. | Elapsed Time=0:00:06 |

Completing error storage...

Overall error storage time: None

Generating XNOR_Logic.LAYOUT_ERRORS...

Generation Time=0:00:00 User=0.01 Sys=0.00 Mem=0.001 GB

Find:

Console

1 First priority errors
0 Second priority errors

Information: Connection established with 'IC Validator VUE' running on 'linux22406.dc.engr.scu.edu'.

Information: Saving design 'Lab4 XNOR Logic schematic'. ([DESIGN_WINDOW-004](#))

Information: Connection closed with 'IC Validator VUE' running on 'linux22406.dc.engr.scu.edu'.

Information:

JobID: icv_drc_2

Completed with no errors.

>